

* Ripple Factor (γ)

The AC components present in the output or DC is known as ripple factor. It is denoted by γ

γ = rms value of ac component value or DC component

$$\gamma = \frac{I_{ac}}{I_{dc}}$$

It should be minimum as possible for effective rectifier

* Mathematical Analysis :-



$$I_{rms} = \sqrt{I_{dc}^2 + I_{ac}^2}$$

$$I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$\frac{I_{ac}}{I_{dc}} = \frac{1}{I_{dc}} \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$\frac{I_{ac}}{I_{dc}} = \frac{1}{I_{dc}} \sqrt{I_{rms}^2 - I_{dc}^2}$$
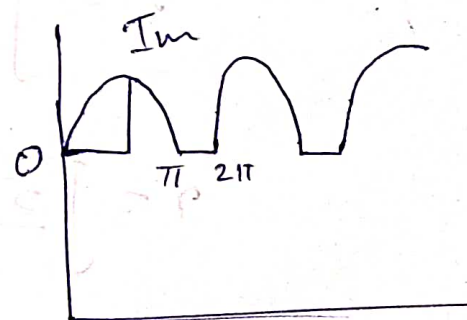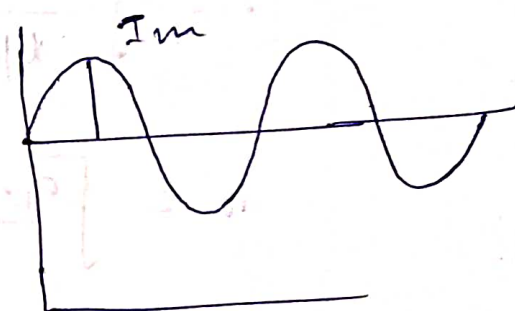
$$= \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1} = \gamma \quad \text{--- (1)}$$



1.

For HWR

$$\left. \begin{aligned} I_{rms} &= \frac{I_m}{2} \\ I_{dc} &= \frac{I_m}{\pi} \end{aligned} \right\} \text{--- (2)}$$

putting the value of (2) in (1)

$$r = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$r = \sqrt{\frac{I_m^2}{2^2(I_m)^2} \times \pi^2 - 1}$$

$$r = \sqrt{\frac{\pi^2}{4} - 1}$$

$$r = \sqrt{\frac{9.8596 - 4}{4}}$$

$$r = \sqrt{\frac{5.8596}{4}}$$

$$r = \sqrt{\frac{1.4649}{1}}$$



$$r = \sqrt{1.4649} = 1.21$$

106/11/23

★ Three types of Transistor configuration

1. CEC \rightarrow Amplifier
2. CBC \rightarrow Impedance
3. CCC \rightarrow RF circuit

★ operating mode of a transistor

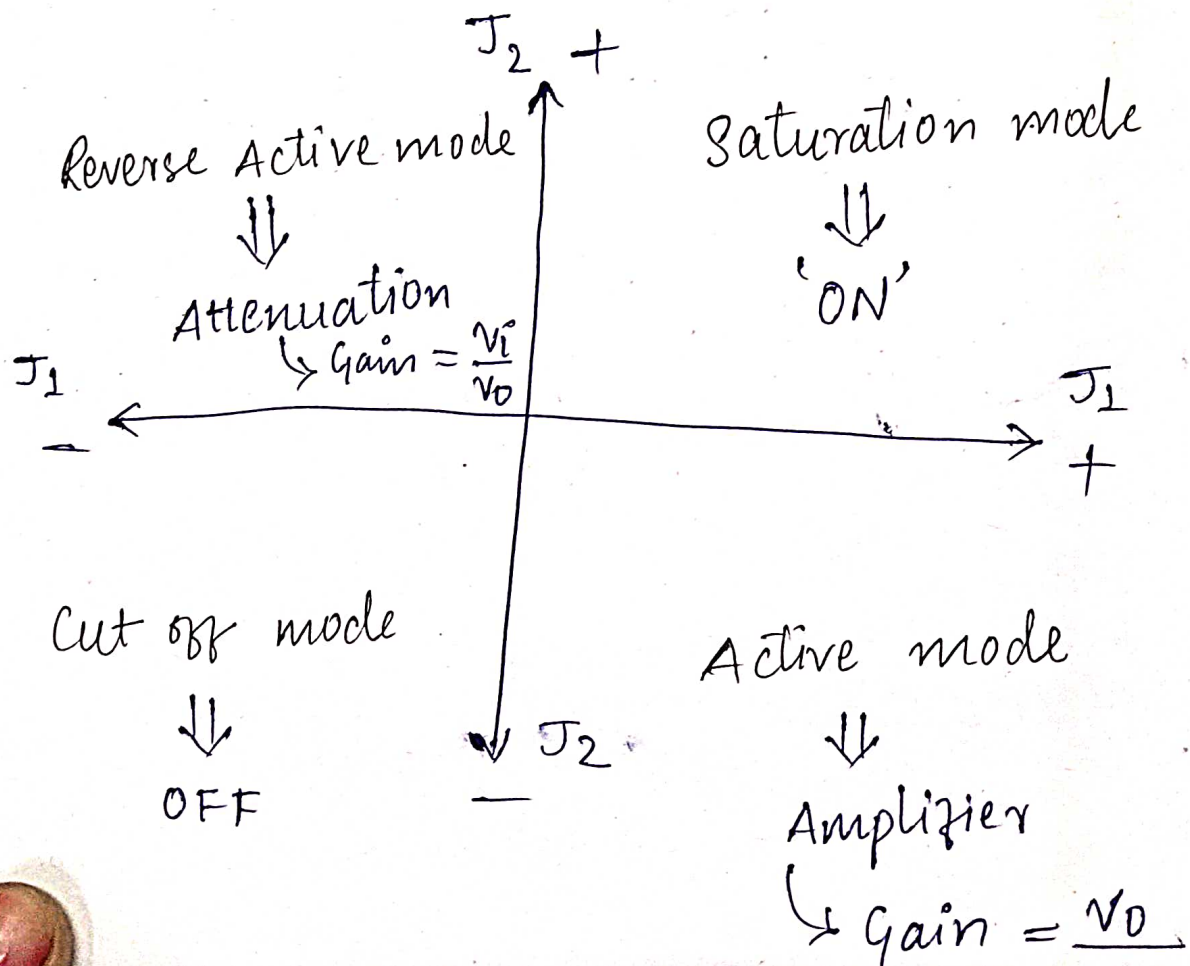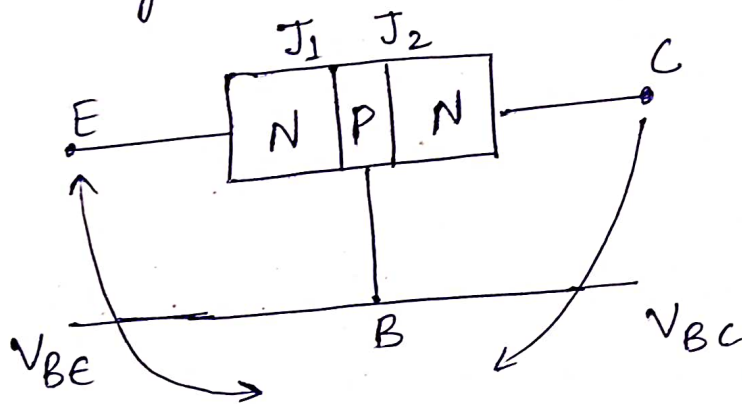

* Characteristics of transistor

Basically, in a transistor three types of characteristics have to be studied namely,


1. Input characteristics
2. Output characteristics
3. Transfer characteristics / Mutual characteristics

* characteristics of transistor in common emitter configuration [CEC]

1. Input characteristics $\rightarrow V_{BE} \text{ Vs } I_B / V_{CE} = \text{const.}$
2. Output $\rightarrow V_{CE} \text{ Vs } I_C / V_{BE} = \text{const.}$
3. Transfer $\rightarrow I_B \text{ Vs } I_C / V_{CE}$

\rightarrow Transistor is current control device
FET (or) voltage control device

Circuit diagram :-

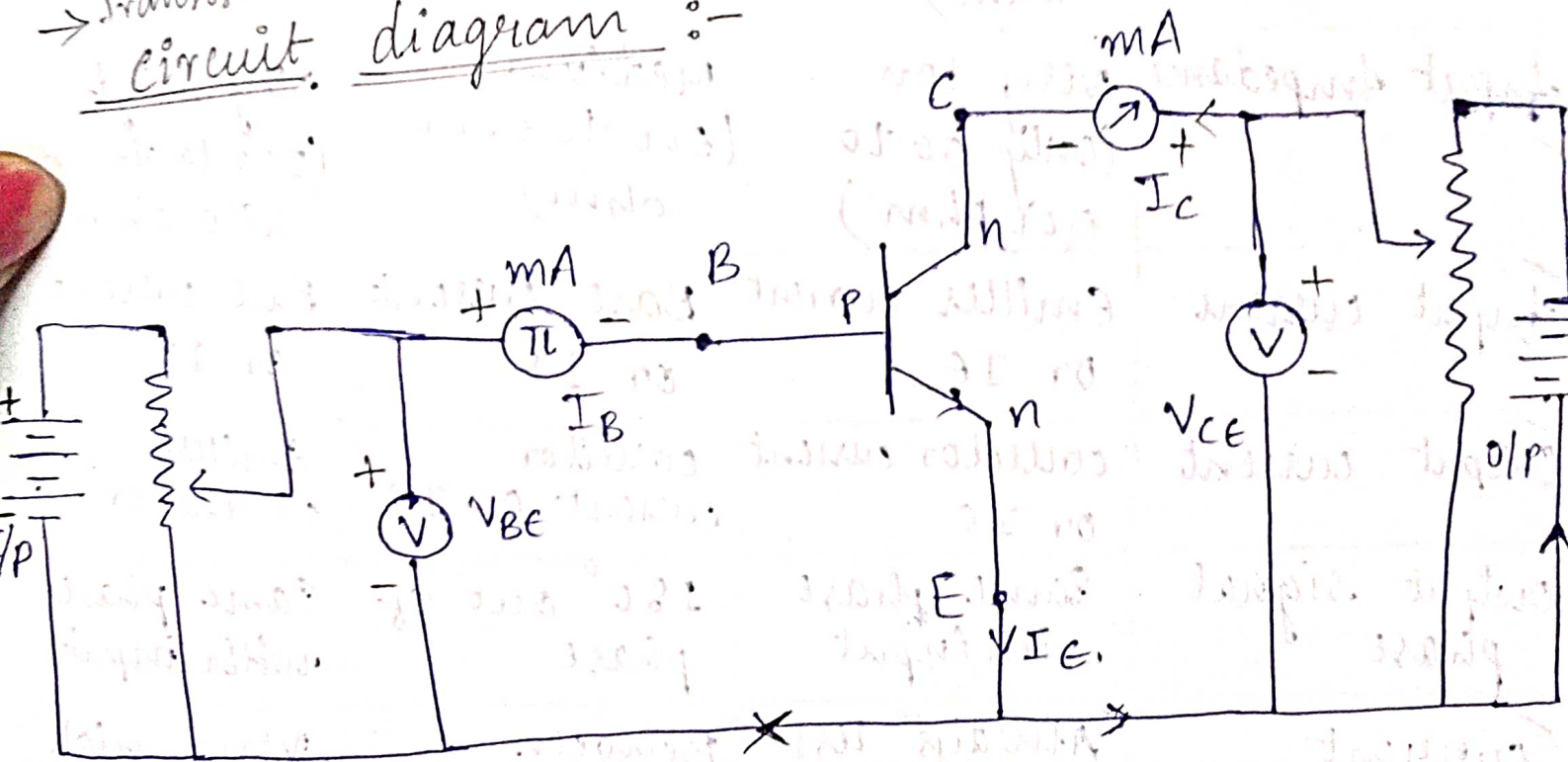

$$I_E = I_B + I_C$$

Assignment


★ compare amount. CBC, CEC and CCC in detail.

| Characteristics | CBC | CEC | CCC |
|---------------------------------------|--|--|---|
| Common terminal for input and output. | Base terminal | Emitter terminal | collector terminal |
| Input voltage applied between | Emitter and Base terminal | Base and emitter terminal | Base and collector terminal |
| Output voltage taken across | collector and Base terminal | collector and emitter terminal | Emitter and collector terminal |
| Output impedance | very high (1 to 10 mega ohm) | Medium (50 to 500 kilo ohm) | very low (up to 50 ohm) |
| Input impedance | very low (only 50 to 500 ohm) | Medium (500 to 5000 ohm) | very high (200 to 750 kilo ohm) |
| Input current | Emitter current or I_E | Base current or I_B | Base current or I_B |
| Output current | collector current or I_C | collector current or I_C | Emitter current or I_E |
| Output signal phase | Same phase with input | 180° out of phase | Same phase with input |
| Current Gain | Always less than unity $\alpha = \frac{I_C}{I_E}$ | Between 35 to 500 $\beta = \frac{I_C}{I_B}$ | very high $\gamma = \frac{I_E}{I_B}$ |


| | | | |
|-----------------|-------------------------|----------------------|--------------------|
| voltage gain | About-150 | About-500 | less than unity |
| leakage current | very small | very large | very large |
| power gain | Medium | High | Medium |
| Application | High frequency circuits | RF signal processing | switching circuits |

08/11/23


1. Input characteristics

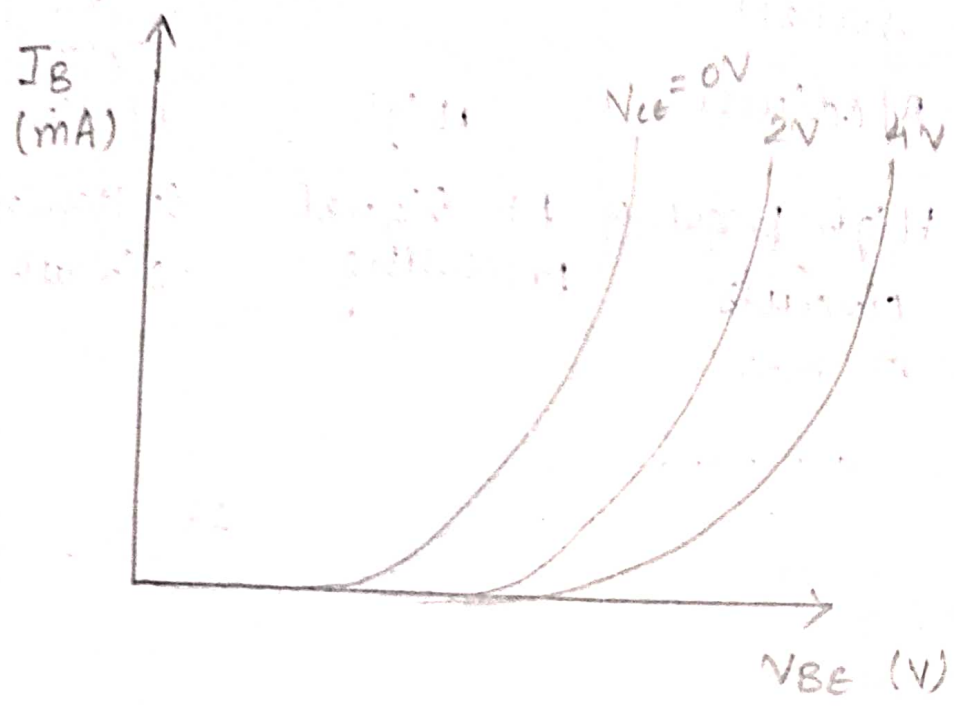

2. Output characteristics

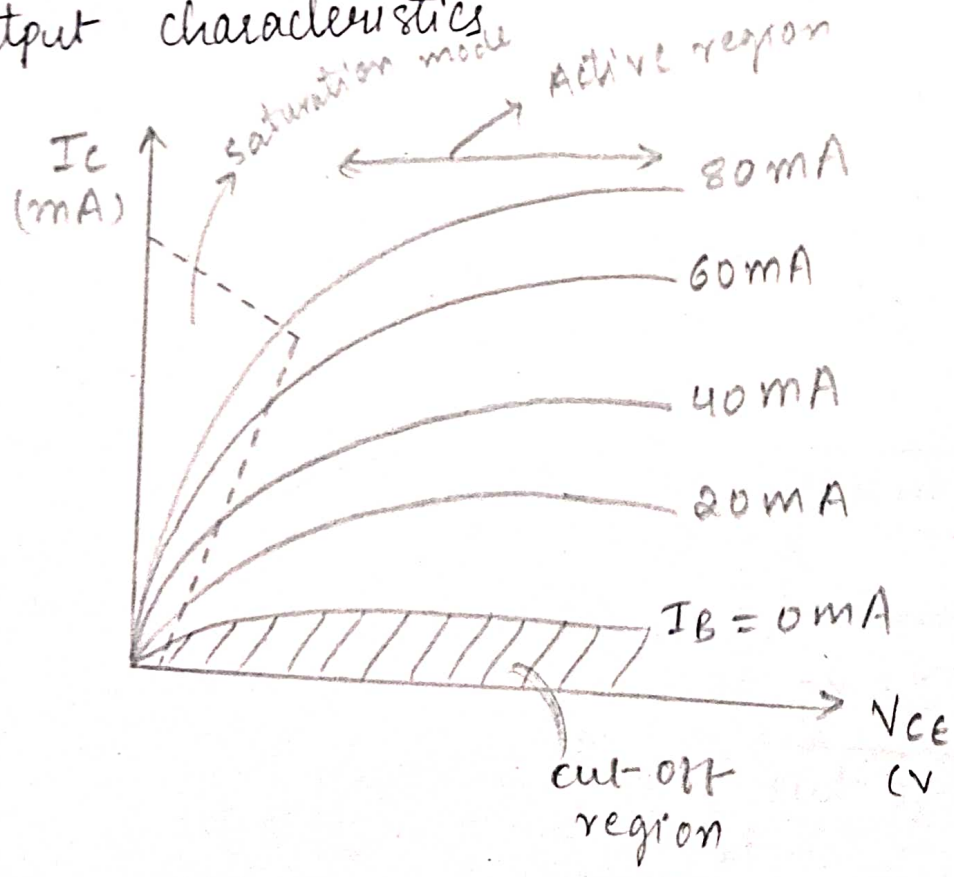

3. Transfer characteristics

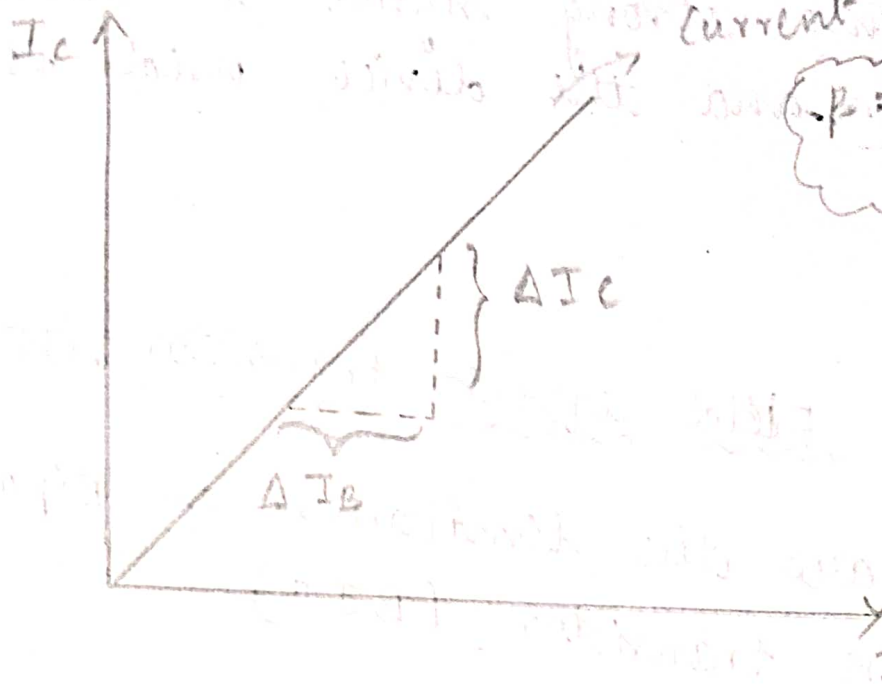

Current gain in CEC

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Home work

- 1) Explain the transistor characteristics in CBC and CCC.
- 2) what is gain of transistor? Reduce the relation among α , β and γ .

$$\alpha \quad \text{CBC} \quad \frac{\Delta I_C}{\Delta I_E}$$

$$\alpha < 1$$

$$\beta \quad \text{CEC} \quad \frac{\Delta I_C}{\Delta I_B}$$

$$\beta > 20-500$$

$$\gamma \quad \text{CCC} \quad \frac{\Delta I_E}{\Delta I_B}$$

$$\gamma \approx 1$$

- 3) How transistor act as a amplifier, explain with proper circuit and example?

1. Amplifier :- the process of increasing with weak signal into strong signal is known as amplification, and the device used is called amplifier.

* Junction Field effect transistor : (JFET)

Que:- what are the limitations of Bipolar junction transistor (BJT).